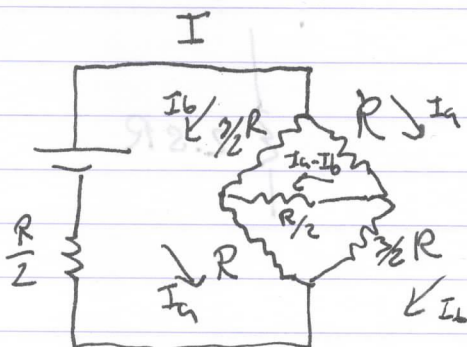


# Solutions to Practice Quiz 5

## Problem 1



By symmetry the currents through Resistances  $R$  must be the same.

Likewise for resistances  $\frac{3}{2}R$ . Also,  $I = I_a + I_b$

We start doing loops.

$$\begin{cases} -I_b \frac{3}{2}R + \frac{R}{2}(I_a - I_b) + R I_a = 0 \\ -(I_b + I_a)\frac{R}{2} + E - R I_a - R \frac{3}{2} I_b = 0 \end{cases}$$

$$\begin{cases} -2I_b + I_a \frac{3}{2} = 0 \\ \frac{3}{2} I_a + 2I_b = \frac{20}{R} = 2 \end{cases}$$

$$3I_a = 2 \rightarrow I_a = \frac{2}{3} \text{ A}$$


(b) Power is additive. Compare loss vs. gain  $I_b = \frac{1}{2} \text{ A}$

$$EI = \frac{R}{2}(I_a + I_b)^2 + 2 \times \frac{3}{2} R I_b^2 + 2R I_a^2 + \frac{R}{2}(I_a - I_b)^2$$

$$EI = (I_a^2 + I_b^2 + 3I_b^2 + 2I_a^2) = R(3(\frac{4}{9}) + 4(\frac{1}{4}))$$

$$20 \frac{7}{6} = 10(\frac{4}{3} + \frac{3}{3}) = 10 \frac{7}{3} \checkmark$$

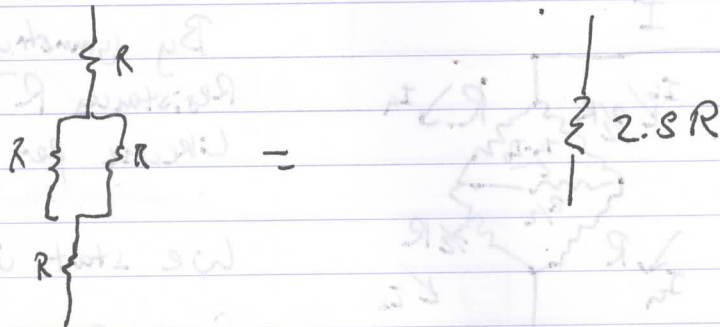Problem 2. Pick the loop that is all batteries  
(plus the resistance you are interested in!).



$$-\mathcal{E} + \mathcal{E} + \mathcal{E} - \mathcal{E} + \mathcal{E} - \mathcal{E} - \mathcal{E} - \mathcal{E} - \mathcal{E} - i2.5R = 0$$

$$-4\mathcal{E} = i2.5R \rightarrow i = \frac{4}{2.5} \frac{\mathcal{E}}{R} = \frac{4}{2.5} \frac{40}{4} = 4A$$

Problem 3.  $S \rightarrow$  student?

$T_0 \rightarrow$  Teacher in

$T_1 \rightarrow$  Teacher ahead

$$\frac{T_0}{S} = \frac{2}{25}$$

$$T_1 = T_0 + 2$$

$$\frac{T_1}{S} = \frac{3}{50}$$

$$T_0 + 2 = \frac{3}{50} S$$

$$T_0 = \frac{2}{25} S$$

$$\left( \frac{2}{25} - \frac{3}{50} \right) S = +2$$

$$S = \frac{+2}{\left( \frac{2}{25} - \frac{3}{50} \right)} = 100$$